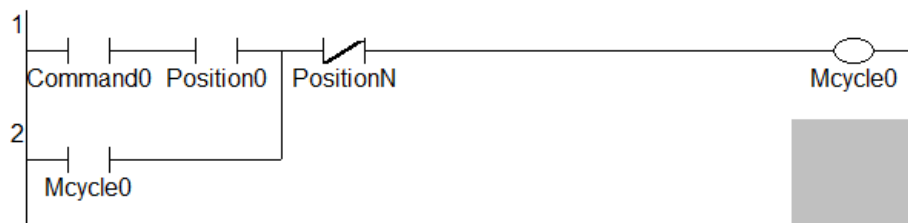



Start/stop ladder circuit problem solving

Start/Stop for cycles and movements

For every distinguishable cycle or stage numbered i on the machine to control, use a start/stop circuit with a mark or memory relay $M_{cycle\,i}$ as output. The cycle is triggered by a combined situation of a $Command\,0$ in this example (it could be a push button) and a start position of the machine, e.g. $Position\,0$. For finishing the cycle, its last $Position\,N$ is evaluated.



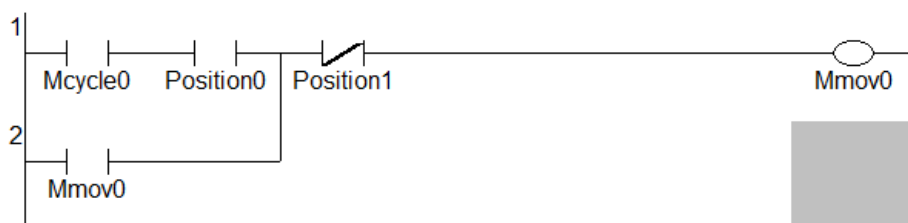When every cycle on the machine to control is distinguished with a memory relay $M_{cycle\,i}$, start to identify every movement in the cycle with a memory relay $M_{mov\,j}$, with its own start and final positions; in this example, $Position\,0$ and $Position\,1$ for memory relay $M_{mov\,0}$.




After that, every memory relay $M_{mov\,j}$ with the same movement as output in the machine, are added to a parallel circuit triggering the real output relay $Q_{mov\,k}$ for that actuator or motor (Move to the Right in this example).




Start/Stop for movements on a sequence

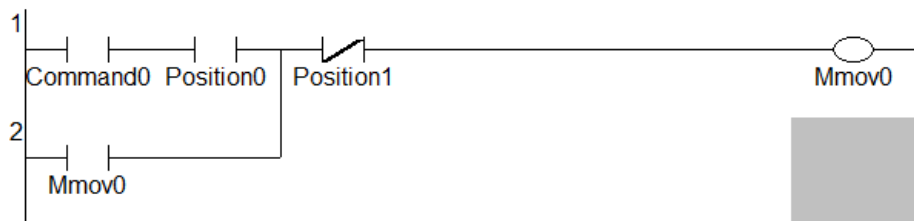Another way of solving sequence of movements on a machine to control, is using first a start/stop circuit for every movement with a memory relay $Mmov_j$ as output. Here as an example, the first order or command $Command0$ (e.g. a push button) combined with the start position $Position0$, triggered memory relay $Mmov0$, until $Position1$ is reached.



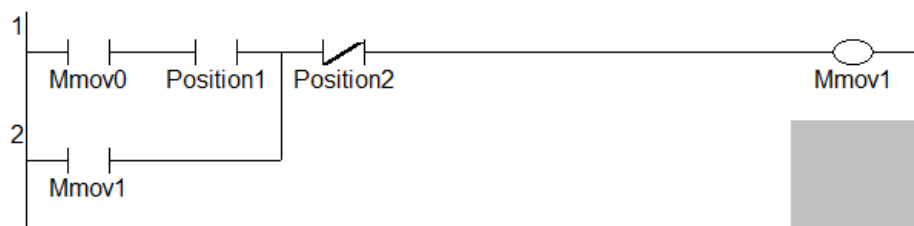Then trigger every movement with the previous one, i.e. $Mmov_j$ combined with the start position of the next movement will trigger its own memory relay $Mmov(j+1)$, until end position for that movement is reached.



After that, every memory relay $Mmov_j$ with the same movement as output in the machine, are added to a parallel circuit triggering the real output relay $Qmov_k$ for that actuator or motor (Move to the Left in this example).



Pablo Cayuela

pablo.cayuela@gmail.com

March 2018